

Step-by-step guide to designing a LL matching network.

- LL matching networks are commonly used to provide broad-band matching.
- Designing a LL network is similar to the π and T networks. You're basically creating two L networks, one for the source side and one for the load side, BUT:
 - o Both L networks will have the same Q value.
 - o Both L networks will be High Ω -Low Ω , (step-down) or both will be Low Ω -High Ω (step-up).
 - o The 'virtual' resistance ' R_V ' replaces R_P for one of the L networks, and R_S for the other.
 - o No components are combined as they are in the π and T networks.
 - o Remember to place the X_P 's next to the LARGER R-value!

NOTE: FOR CONVENTION CONSISTENT WITH CLASSROOM MATERIALS, THE FOLLOWING NOMENCLATURES ARE USED:

- X_{S1} , X_{P1} ARE THE LEFT SIDE SERIES AND PARALLEL REACTANCES, RESPECTIVELY
- X_{S2} , AND X_{P2} REPRESENT THE RIGHT, (TYPICALLY LOAD-SIDE)SIDE VALUES

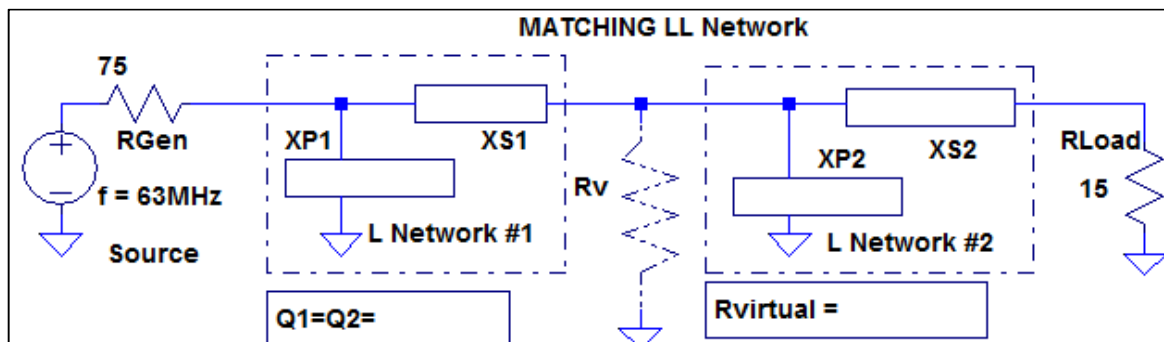


Figure 1. Matching LL Network Template. This one is a step-down example, where $R_{Gen} > R_V > R_{Load}$. In a step-up network, X_{P1} and X_{P2} would be to the right of X_{S1} and X_{S2} ...

STEPS:

1. Calculate the virtual resistance value R_V :
 - R_V is simply the square root of the product of R_S and R_P :


$$R_V = \sqrt{R_{gen} * R_{Load}} \quad \text{In our example: } R_V = \sqrt{75 * 15} = 33.54\Omega$$
2. Calculate Q using the Q formula: $Q_1 = \sqrt{R_P/R_S - 1}$. In the example, note that the example is a step-down matching network, ($R_{gen} > R_V > R_{load}$). So R_{gen} is used in place of R_P , and R_V is used in place of R_S :

$$Q_1 = \sqrt{R_{gen}/R_V - 1} = \sqrt{75/33.54 - 1} = 1.112$$

3. Calculate the reactances using R_V , and Q, and R_{GEN} for the source side, and R_{LOAD} for the load side.

$$X_S = \pm Q * R_S \quad X_P = \pm R_P / Q$$

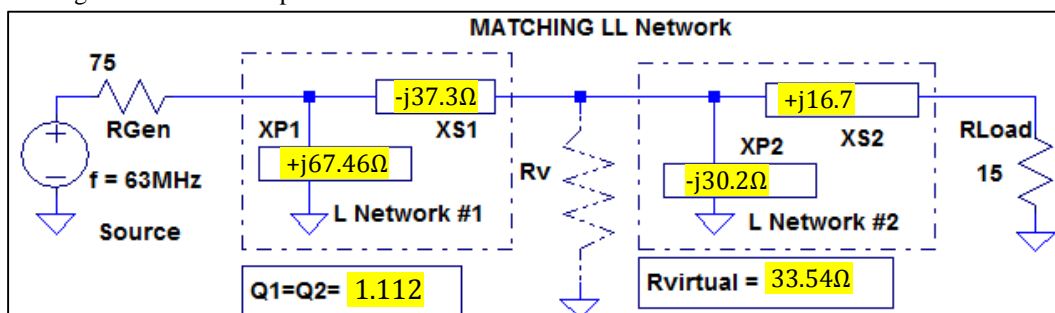4. Determine whether you want HI-pass or LO-pass filters for each L network and assign $\pm j$'s accordingly. Values for a HI/LO arrangement of the example are shown here:



5. Use AC analysis to verify your work. The total impedance load seen by the generator should be equal to its source impedance.

REFERENCE MATERIAL: BOWICK, PGS. 63 - 72